

# ECE 3 Lab 1 prelab

Lawrence Liu

March 28, 2022

## Problem 1

(a)

$47k\Omega$  with variance of 5%

(b)


$100k\Omega$  with variance of 10%

## Problem 2


$0\Omega$  because the resistor is parallel with a short circuit, to properly measure the resistance you should plug in the resistor with B one row back.

## Problem 3


**Ideal Voltage Source**

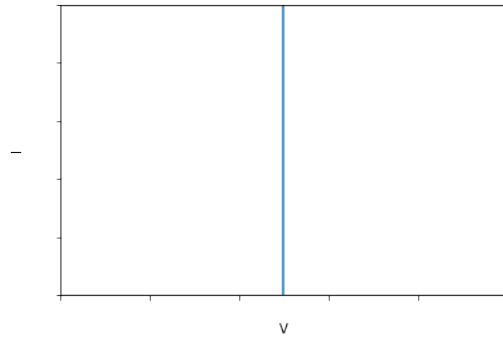


**Non Ideal Voltage Source**

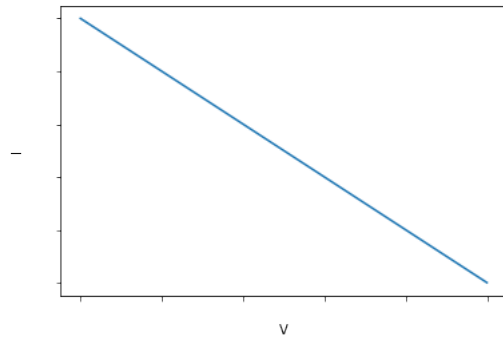

**Ideal Current Source**

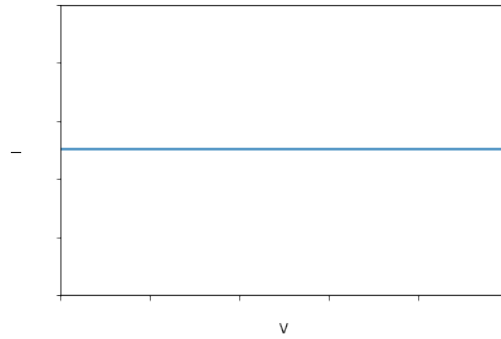

## Non Ideal Current Source

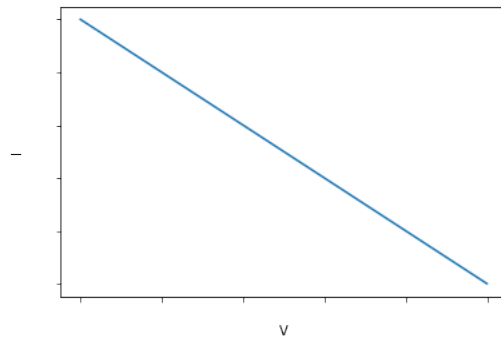

## Problem 4

### Voltage Divider

From KVL we have

$$V_0 = I(R_1 + R_2)$$

$$I = \frac{V_0}{R_1 + R_2}$$

therefore we have that the voltage drop across  $R_1$  is

$$\frac{V_0 R_1}{R_1 + R_2}$$

## Voltage Divider

We have

$$V_0 = I_T \frac{R_1 R_2}{R_1 + R_2}$$

therefore we have that the current across  $R_1$  is

$$V_0 = I_1 R_1$$

$$I_T \frac{R_1 R_2}{R_1 + R_2} = I_1 R_1$$

$$I_T \frac{R_2}{R_1 + R_2} = I_1$$