

EE3 Spring 2022

Homework Problem 4

Use the $V_{oc} - I_{sc}$ method to find the Thévenin Equivalent circuit looking into the port defined by the two open circle terminals.

