

ECE 3 HW 7

Lawrence Liu

May 11, 2022

We have that

$$I_{body} = \frac{120.001}{400M + 200k} = 299.852nA$$

Therefore we must have

$$V_{s-} = 59.970V$$

and

$$V_{s+} = 60.031V$$

From virtual short principle we must have $V_{s-} = V_2$ and $V_{s+} = V_1$, therefore from the voltage divider principle we must have that $v_n = v_p = 54.518V$ for the right most op amp. Therefore we must have that the current flowing across the upper 10k ohm resistor is

$$V_{s+} - v_p 10k = 0.551A$$

Therefore we must have that that

$$V_o = \boxed{-609mV}$$